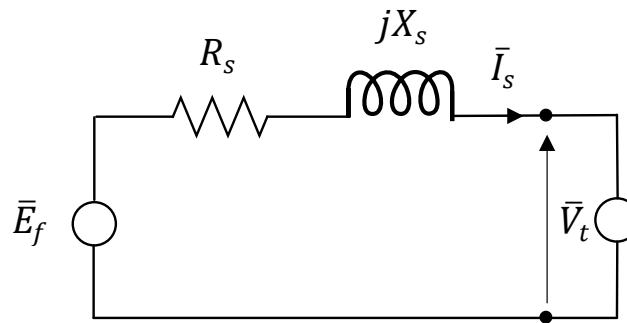


Problem 1 (20 points)

A three phase 60 Hz synchronous motor has four poles. The motor rated voltage is 460 V/266 V wye. Equivalent stator impedance $X_s = 1.5 \Omega$ and $R_s = 0.05 \Omega$. The motor rated stator current is 180 A. The motor internal voltage is $E_f = 30I_f$, where I_f is the motor field current. The per phase equivalent circuit is shown below.




Develop the V curve for this motor under the real power consumption of 120 kW, plotting stator current as a function of field current using MATLAB. Include **at least five data points** in the V curve.

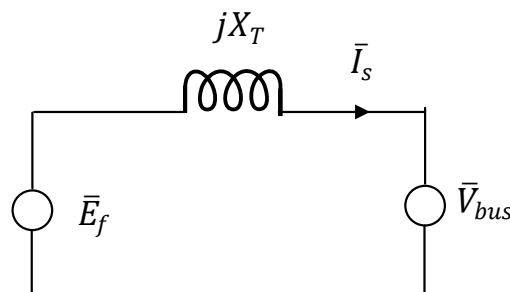Problem 2 (20 points)

A three phase, four pole 60 Hz synchronous generator is rated at 1000 MVA and 22.5 kV/13 kV wye. The generator synchronous reactance $X_s = 0.7 \Omega$. The generator is feeding into a system that has system equivalent reactance $X_{sys} = 0.1 \Omega$ and infinite bus voltage of 13.0 kV line to neutral.

- The generator internal voltage $E_f = 19.5$ kV line to neutral. Determine P_{max} for this operating point.
- The generator is delivering 700 MW to the infinite bus. Determine the angle δ of the generator internal voltage.
- Determine the generator terminal voltage V_t .
- Determine the VAR flow at the generator terminal for this operating point.
- The generator power decreases to 200 MW. Determine the new value of the power-angle δ .



Problem 3 (20 points)

A three-phase, 8-pole, 75 HP squirrel cage induction motor has the following characteristics:

$R_1 = 0.05 \Omega$	$X_1 = 0.2 \Omega$	$X_m = 10 \Omega$
$R'_2 = 0.055 \Omega$	$X'_2 = 0.2 \Omega$	

The motor is operating at a speed of 875 rpm with a terminal voltage of 460V/266V – 60 Hz.

- Calculate the motor slip.
- Calculate the stator current \bar{I}_1 and the rotor current \bar{I}'_2 . Assume that the motor terminal voltage is at 0° for this calculation.
- Calculate the motor efficiency
- Calculate the developed torque of the motor T_e .

Problem 4. (20 points)


The previous motor in problem 3 is fed from a source with an open circuit voltage of 277 V at the frequency of 50 Hz and a source impedance of $Z_{th} = 0.04 + j0.11 \Omega$. Determine the motor terminal voltage, stator current and torque at motor starting $s = 1$ and at the motor's rated speed.

Problem 5. (20 points)

An 8-pole doubly fed induction generator (with the below equivalent circuit) has the following parameters

$R_1 = 0.05 \Omega$	$L_1 = 1 \text{ mH}$	$L_m = 200 \text{ mH}$
$R_2 = 0.01 \Omega$	$L_2 = 0.3 \text{ mH}$	$a = 2$

- With the input frequency of 60 Hz, the generator is operating at the speed of 1850 rpm. Determine the slip of the generator
- The generator is operating with a stator line to neutral voltage of $V_1 = 2400\text{V}$. The stator winding is delivering 1.5 MW at 20 degree lagging power factor to the grid. Determine the value of the current I_1 .
- Solve the per phase equivalent circuit to find the rotor voltage and current.
- Find the real and reactive power flowing out of the rotor.

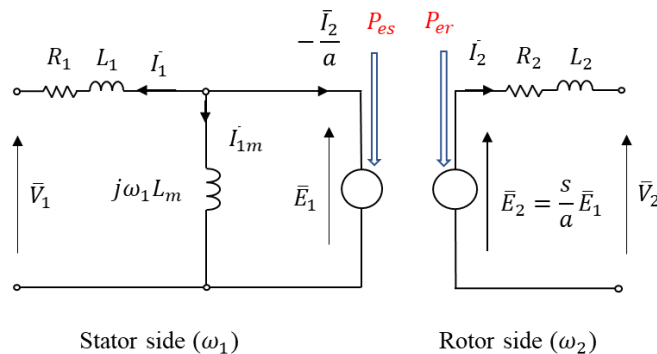

Equivalent circuit of double-fed
induction machine