

## EE331 Fall 2019 HW 1

Lewis Collum

Updated: September 18, 2019

---

### 1

Q1: Find the phasor current  $I_S$

```
v = {'S': 120}

z = {
    'M': 10 + 4j,
    'S': 0.2 + 0.5j,
    'L': 0.3 + 0.1j,
    'X': 3 + 10j
}

z['LM'] = z['L'] + z['M']
z['LMX'] = (z['LM']**(-1) + z['X']**(-1))**(-1)
z['equivalent'] = z['LMX'] + z['S']

i = {'S': v['S']/z['equivalent']}
print("\n(\\boxed{I_S =", f"{i['S']:.3}", "\\si{A}}\\)")
```

$$I_S = (11.9 - 14.2j)A$$

Q2: Find the phasor voltage  $V_X$

$$\begin{aligned}\frac{V_S - V_X}{Z_S} &= I_S \\ \Rightarrow V_X &= V_S - Z_S I_S\end{aligned}$$

```
v['X'] = v['S'] - i['S']*z['S']
print("\n(\\boxed{V_X =", f"{v['X']:.3}", "\\si{V}}\\)")
```

$$V_X = (111 - 3.12j)V$$

Q3: Find active power, reactive power, and apparent power flows at point X

```
p = {'X': v['X']*i['S']}
p['apparent'] = abs(p['X'])
p['active'] = p['X'].real
p['reactive'] = p['X'].imag
print(f"Active Power @ X = {p['active']:.5} W")
print(f"Reactive Power @ X = {p['reactive']:.5} W")
print(f"Apparent Power @ X = {p['apparent']:.5} W")
```

Active Power @ X = 1272.7 W

Reactive Power @ X = -1604.0 W

Apparent Power @ X = 2047.5 W

---

### 2

---

### 3

---

### 4