

EE 331 Homework Set 5 (Due at 11AM on October 30th, 2019)

Problem 1 (15 points) (5 points each question)


A three phase eight pole 60 Hz wye connected synchronous generator is rated at 2.50 MVA, 4.16/2.4 kV. The generator has a stator resistance of $R_s = 0.15 \Omega$ and a synchronous reactance of $X_s = 4.0 \Omega$.

- Find the rated stator current of the generator
- The generator is operating at rated terminal voltage with rated current. The current is lagging the line to neutral voltage by 25° . Find the internal voltage E_f of the generator.
- Find the converted power and the developed torque T_e .

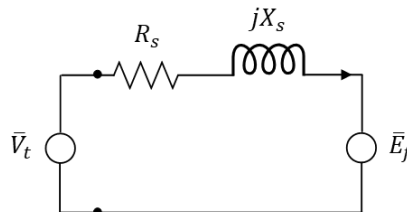Problem 2 (15 points) (5 points each question)

A three phase 60 Hz synchronous motor has eight poles. The motor rated voltage is 480V/277V wye. The motor rated stator current is 300 A. The per-phase diagram of the motor is shown below with $R_s = 1 \Omega$, $X_s = 0.2 \Omega$. The motor is operating with a terminal voltage magnitude of $V_t = 282$ V with a frequency of 60 Hz. The current magnitude $I_s = 200$ A. I_s is in phase with V_t .

- Calculate the magnitude and angle of the internal voltage E_f .
- The internal voltage magnitude $E_f = 0.075\omega_e I_f$, where ω_e is the electrical frequency in radians per second, and I_f is the field current. Find the field current for this operating point.
- The converted power for the motor is the real power entering the internal voltage source E_f . Find the converted power for this motor. Find the developed torque of the motor.



Equivalent circuit.

Problem 3 (20 points) (5 points each question)

The motor of problem 2 is operating with a developed torque of $T_e = 500$ N m and a field current of $I_f = 20$ A. The electrical frequency is 60 Hz.


- Determine the internal voltage E_f .
- Calculate the converted power P_e .
- Assume that the stator current is in phase with the internal voltage. Determine the stator current magnitude I_s and calculate the motor terminal phasor voltage V_t .
- Calculate the terminal real power P_t and reactive power Q_t .

Problem 4 (20 points) (5 points each question)

A 32-pole 60 Hz synchronous turbine generator has 150 MW shaft power. It has a stator copper loss of 0.5 MW, friction and windage loss of 5 MW, electromagnetic losses of 1.5 MW and field winding and cooling losses of 2.1 MW. The generator is operating with electrical frequency of 60 Hz.

- Determine the rotor speed of the generator in (revolutions per minute) RPM and in rad/s. Determine corresponding mechanical torque T_m .

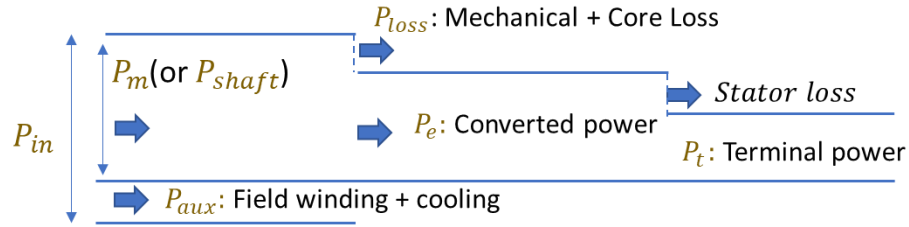- Calculate the magnitude of the stator current I_s if $R_s = 0.2 \, \Omega$.
- Using the power flow diagram as shown below, determine the converted power P_e of the machine, and the developed torque T_e .
- Determine the terminal power and overall efficiency of the generator at this operating point.



Power flow diagram.

Problem 5 (20 points) (5 points each question)


A three phase, four pole 60 Hz synchronous generator is rated at 800 kVA, 440 V/254 V wye. The generator synchronous reactance $X_s = 0.8 \, \Omega$ and the stator resistance is $R_s = 0.004 \, \Omega$. The generator internal voltage magnitude is $E_f = 0.035\omega_e I_f$. The field resistance is $R_f = 8 \, \Omega$. The generator is operating at 60 Hz.

- The generator is initially supplying power to a wye connected load with impedance of $Z_{wye} = 1.2 + j0.3 \, \Omega$. The terminal voltage is $V_t = 270V$. Determine the stator current from the per phase diagram.
- Determine the internal phasor voltage \bar{E}_f .
- Find the field current and the field voltage that will provide this value of E_f .
- A new load is added in parallel to the original load. The impedance of this load is $Z_{wye2} = 1.8 + j0.5 \, \Omega$. The value of \bar{E}_f remains the same. What is the new phasor terminal voltage \bar{V}_t ?

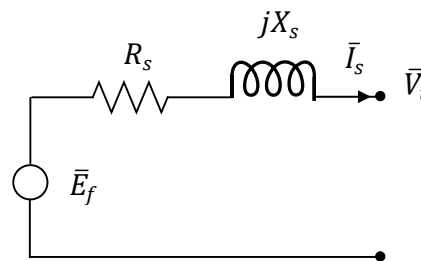Problem 6 (10 points) (5 points each question)

The per phase diagram of a synchronous generator connected to an infinite bus is shown below. The generator has a stator resistance of $R_s = 0.05 \, \Omega$ and a synchronous reactance of $X_s = 4.0 \, \Omega$. The generator is a wye connected 66 MVA, 60 Hz 32-pole machine driven by a hydraulic turbine. The generator is operating with a terminal voltage of 13.2 kV L-L (7.62 kV L-N). The generator is operating with rated output volt-amps at an 0.85 lagging power factor. The system frequency is 60.0 Hz.

- Find the phasor values of internal voltage \bar{E}_f and phase current \bar{I}_s .
- Find the generator shaft speed and developed torque.



Equivalent circuit.