

## EE331 Fall 2019 HW 8

Lewis Collum

Updated: November 26, 2019

---

(1)

First we encapsulate values that are given in python dictionaries.

```
import numpy
import matplotlib.pyplot as pyplot
import pint
unit = pint.UnitRegistry()

terminal = {
    'power': 120 * unit.kW,
    'voltageRated': 266 * unit.V
}

stator = {
    'currentRated': 180 * unit.A,
    'impedance': (0.05 + 1.5j) * unit.ohms
}

field = {}
```

We are assuming the motor is running at its rated voltage. With this assumption, we get the current through the stator.

```
stator['current'] = (terminal['power']/3/terminal['voltageRated']).to('A')
print(f"\(I_s = {stator['current']:.2fLx}\)")
```

$I_s = 150.38 \text{ A}$

Since we know the rated current, we can find out the max imaginary stator current.

```
stator['currentMaxImaginary'] = numpy.sqrt(stator['currentRated']**2 - stator['current']**2)
print(f"\(\max\{(I_m(I_s))\} = {stator['currentMaxImaginary']:.2fLx}\)")
```

$\max(I_m(I_s)) = 98.93 \text{ A}$


We will use the max imaginary current to establish a range for our v-curve.

```
imaginaryRange = 1j*stator['currentMaxImaginary'] * numpy.linspace(-1, 1, 21, endpoint=True)
stator['currents'] = stator['current'] + imaginaryRange
```

Now we can calculate the field current,  $I_f$ , for each stator current in our `stator['currents']` array.

```
field['voltages'] = (stator['currents']*stator['impedance'] + terminal['voltageRated']).to('V')
field['currents'] = (abs(field['voltages']) / (30*unit.ohms)).to('A') #Given in problem statement
```

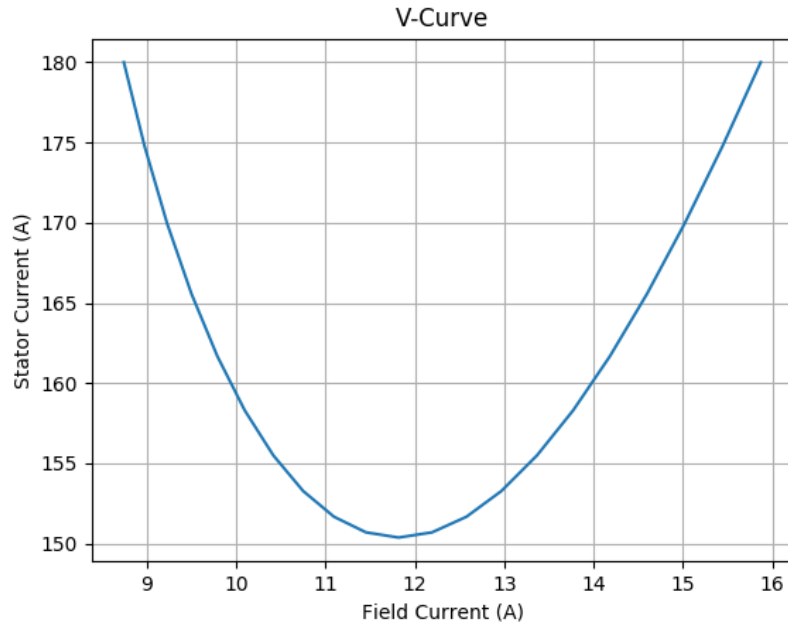Finally, we plot stator currents vs field currents.



(2)

**(a) Find  $P_{max}$  at  $E_f = 19.5\text{kV}$**

Assuming  $R_s, R_{sys} \ll X_{sys} \ll X_s$ :

$$X_T = X_s + X_{sys} = 0.80 \Omega$$

And, given:

$$V_{bus} = 13.00 \text{ kV}$$

$$E_f = 19.50 \text{ kV}$$

The maximum output power of the generator is obtained when  $\delta = 90^\circ$ .

$$P_{e,max} = \frac{3E_f V_{bus}}{X_T} \sin 90^\circ = \boxed{950.63 \text{ MW}}$$

**(b)**

$$\delta = \sin^{-1} \frac{700 \text{ MW}}{P_{e,max}} = \boxed{47.42^\circ}$$

**(c)**

We apply the current  $\delta$  to the field voltage at  $\delta = 90^\circ$  to get  $E_f$ .

$$E_f = 19.50 \angle 47.42^\circ \text{ kV}$$

Now, to get the stator current,  $I_s$ ,

$$E_f = I_s \cdot X_T + V_{bus}$$

$$\rightarrow I_s = \frac{E_f - V_{bus}}{X_T} = 17.95 \angle -0.77^\circ \text{ kA}$$

Finally, we get the terminal voltage,  $V_t$ .

$$V_t = I_s \cdot X_{sys} + V_{bus}$$

$$V_t = \boxed{14.79 \angle -0.09^\circ \text{ kV}}$$

(d)

$$S_t = (796.66 + 9.44i) \text{ MVA}$$

$$Q_t = \boxed{9.44 \text{ MVAR}}$$

(e)

$$\delta = \sin^{-1} \frac{200 \text{ MW}}{P_{e, \max}} = \boxed{12.15^\circ}$$

---

(3)

(a) Calculate Motor Slip

$$s = \frac{\omega_2}{\omega_1} = \frac{\omega_1 - p_p \omega_r}{\omega_1}$$

$$\omega_1 = 376.99 \text{ rad s}^{-1}$$

$$\omega_r = 91.63 \text{ rad s}^{-1}$$

$$s = \frac{\omega_1 - p_p \omega_r}{\omega_1} = \boxed{0.03}$$

(b)  $I_1, I_2$

$$Z_{eq} = R_1 + jX_1 + \left(\frac{R'_2}{s} + jX'_2\right) || jX_m = (1.88 + 0.75i) \Omega$$

$$I_1 = \frac{V_1}{Z_{eq}} = \boxed{131.13 \angle -21.76^\circ \text{ A}}$$

$$E_1 = 251.15 \angle -5.01^\circ \text{ V}$$

$$I'_2 = \frac{E_1}{R'_2/s + jX'_2} = \boxed{126.20 \angle -10.78^\circ \text{ A}}$$

(c) Motor Efficiency

$$P_1 = \Re(3V_1 I_1^*) = 97.18 \text{ kW}$$

$$P_{es} = \Re(3E_1 I_2'^*) = 94.60 \text{ kW}$$

$$P_m = (1 - s)P_{es} = 91.97 \text{ kW}$$

$$\eta = \frac{P_m}{P_1} = \boxed{0.95}$$

(d)

Assuming no mechanical loss,  $P_e = P_m$

$$T_e = \frac{P_e}{\omega_r} = \boxed{1.00 \text{ kW s rad}^{-1}}$$

---

(4)

$$Z_{eq} = R_1 + jX_1 + \left(\frac{R'_2}{s} + jX'_2\right) || jX_m + Z_{th} = (0.14 + 0.51i) \Omega$$

$$I_1 = \frac{V_{src}}{Z_{eq}} = \boxed{526.48 \angle -74.24^\circ \text{ A}}$$

$$V_t = V_{src} - I_1 Z_{th} = \boxed{215.59 \angle 1.21^\circ \text{V}}$$


---

(5)

**(a) Slip**

$$\omega_1 = 376.99 \text{ rad s}^{-1}$$

$$\omega_r = 193.73 \text{ rad s}^{-1}$$

$$\omega_2 = -397.94 \text{ rad s}^{-1}$$

$$s = \boxed{-1.06}$$